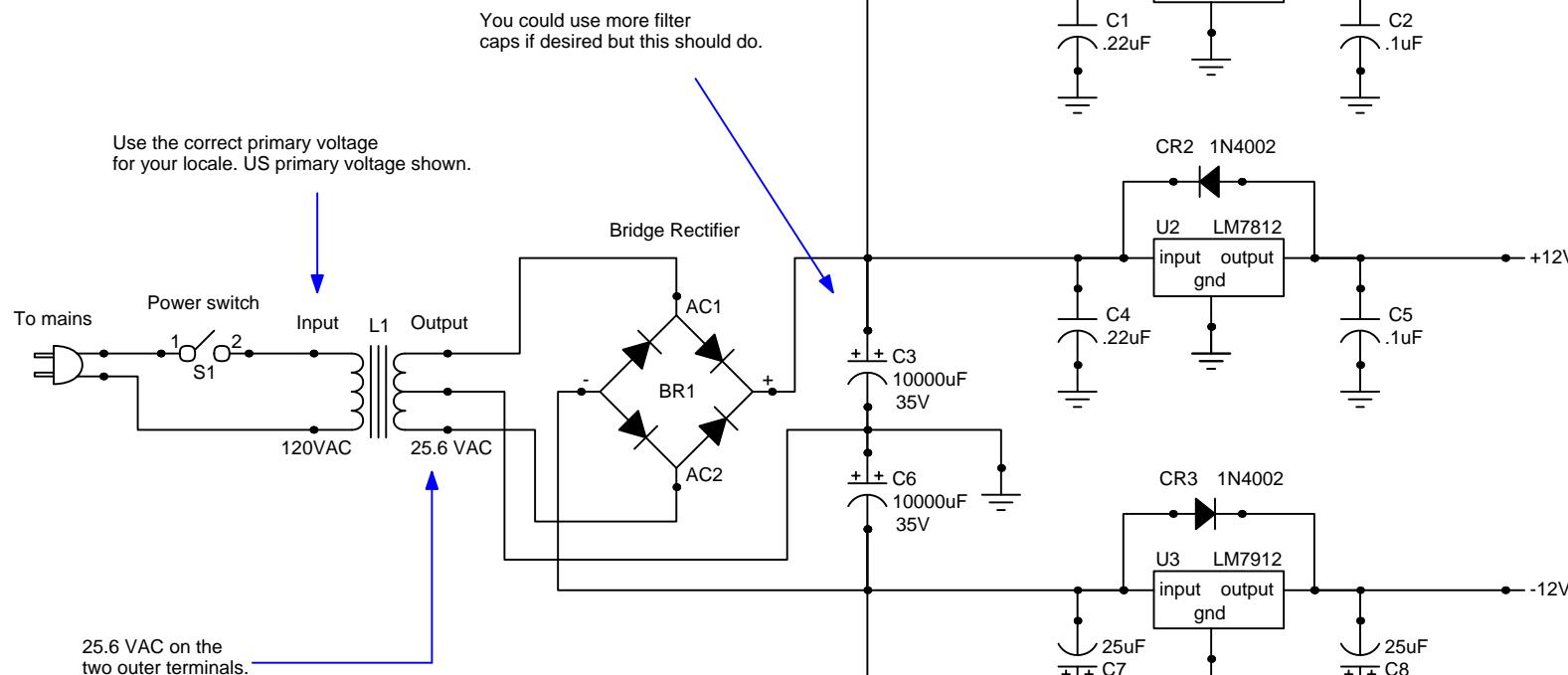


Multi-Output Voltage Supply Using LM78XX/LM79XX Voltage Regulators.

Drawn by Ray Wilson


Caps and diodes suggested by National Semiconductor.



*** IMPORTANT NOTES ***

DO NOT SHORT TABS OF REGULATORS USE SEPARATE HEAT SINKS!!

LM78XX Pin Orientation

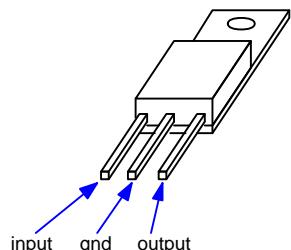

LM79XX Pin Orientation

