



You can use 2 matched general purpose NPN transistors in place of U3 (LM394). If you don't have matched transistors 2 - 2N3904s will work to get you making sound (and may just work fine too).

You can choose to eliminate R11 and just add a wire to short across it. It may make 1V/Octave adjustments far simpler due to the fact that R11 and R16 will interact and may drive you mad.

